
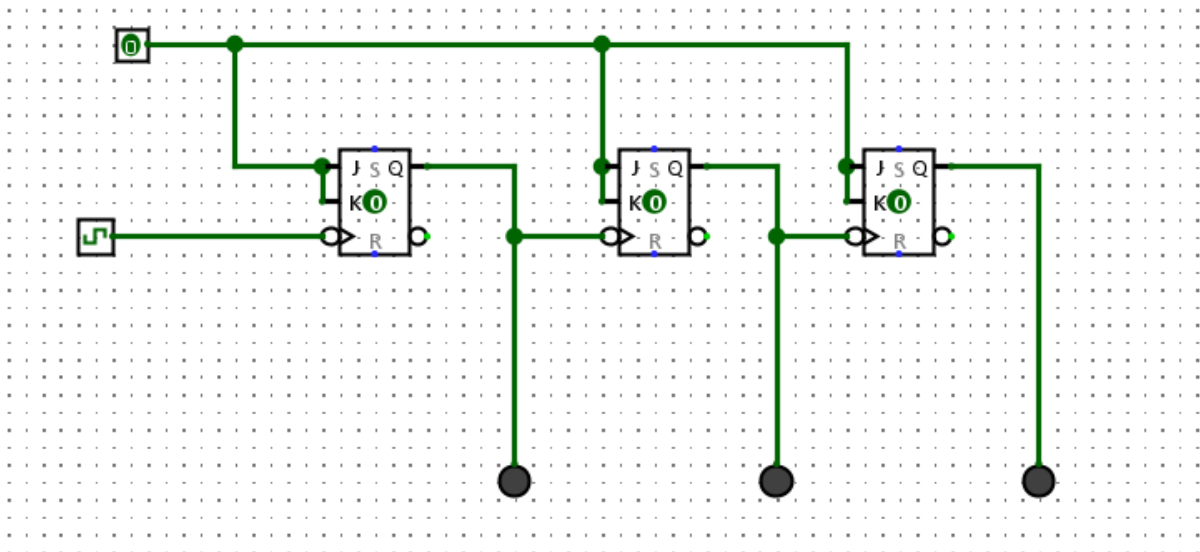



3-Bit Ripple Counter

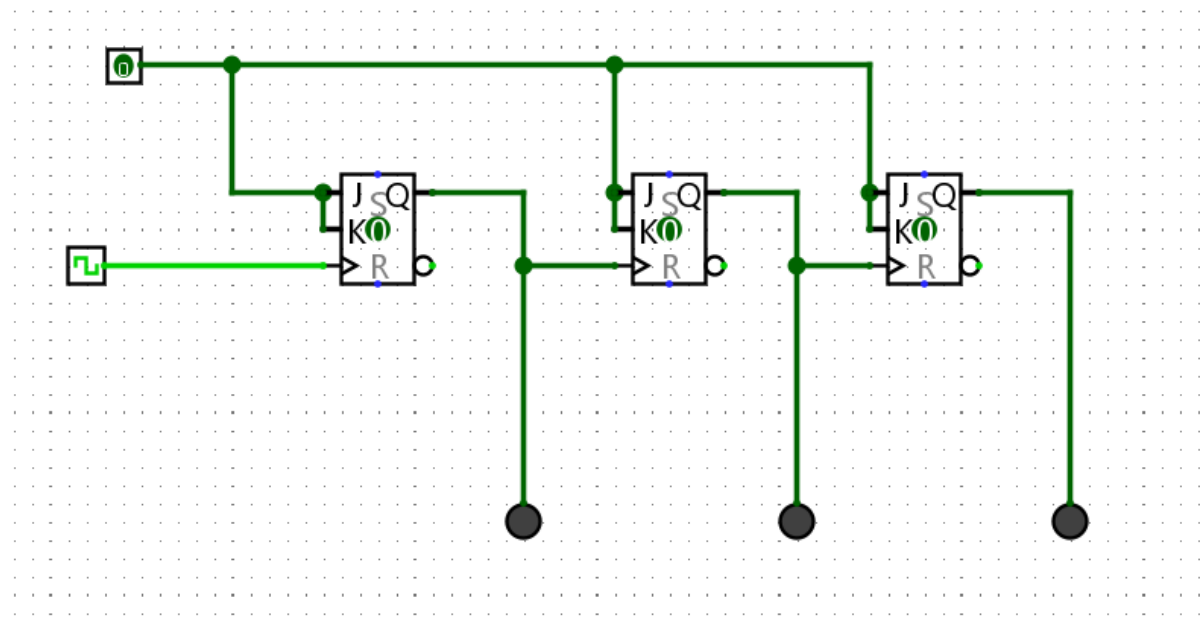


3-Bit Count-down Ripple Counter



3-Bit Common-Clock Counter

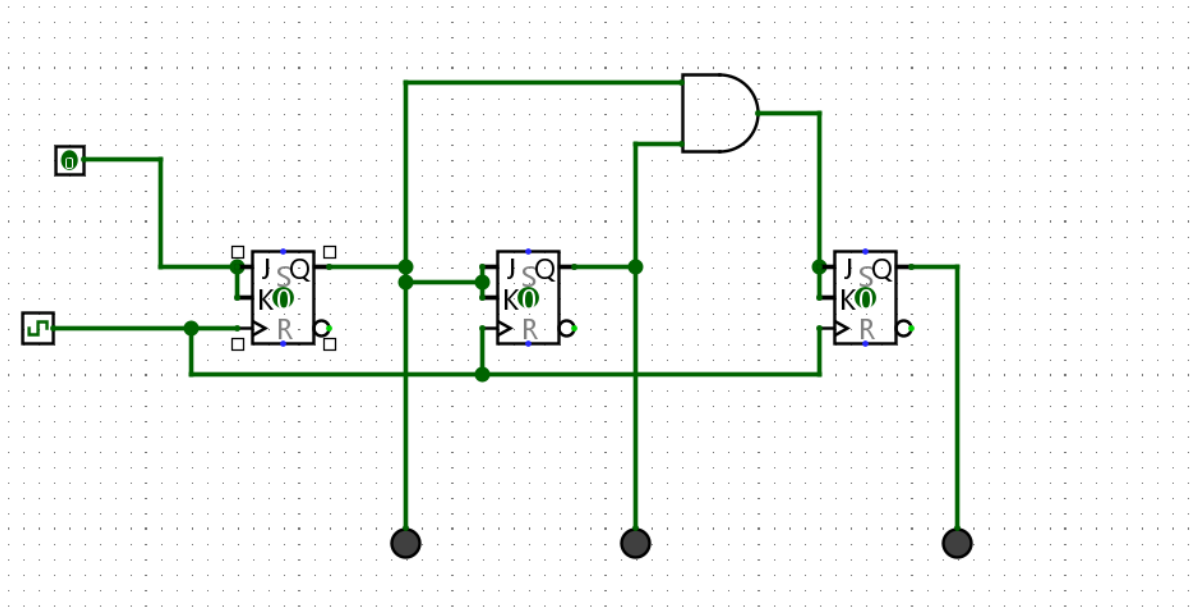

3-Bit Common-Clock MOD 6 counter

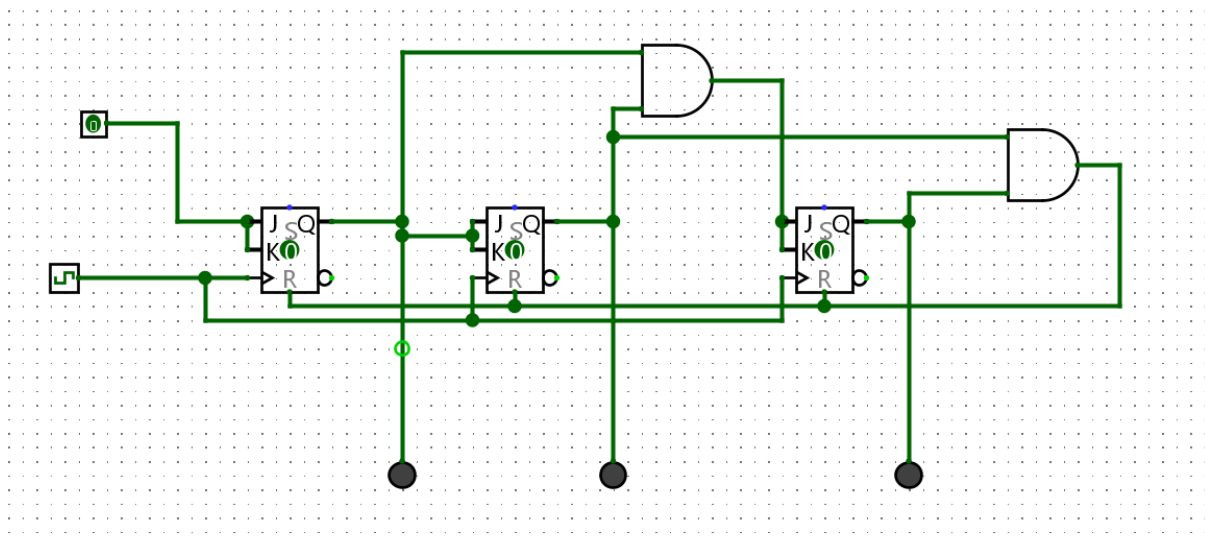

3-Bit MOD 6 No illegal state counter with HEX Display

